

# *Digital Integrated Circuits*

## *A Design Perspective*

Jan M. Rabaey  
Anantha Chandrakasan  
Borivoje Nikolic

# Semiconductor Memories

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## *Chapter Overview*

- ☐ **Memory Classification**
- ☐ **Memory Architectures**
- ☐ **The Memory Core**
- ☐ **Periphery**
- ☐ **Reliability**
- ☐ **Case Studies**

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## Semiconductor Memory Classification

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## Memory Timing: Definitions

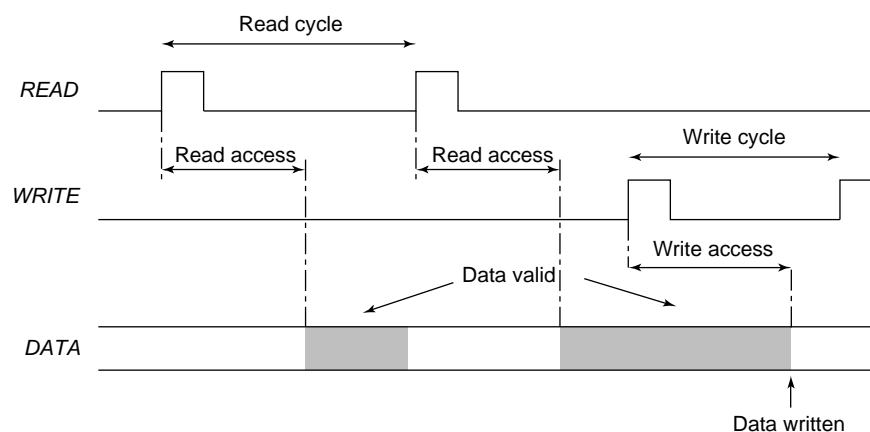

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Memory Architecture: Decoders

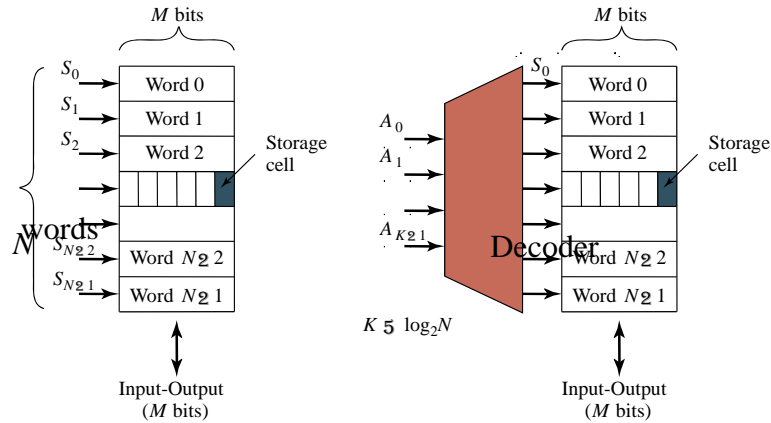

Intuitive architecture for  $N \times M$  memory  
Too many select signals:  
 $N$  words ==  $N$  select signals


Decoder reduces the number of select signals  
 $K = \log_2 N$

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Array-Structured Memory Architecture

 
Problem: ASPECT RATIO or HEIGHT  $\gg$  WIDTH



© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Hierarchical Memory Architecture

 


### Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block  $\Rightarrow$  power savings

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Block Diagram of 4 Mbit SRAM

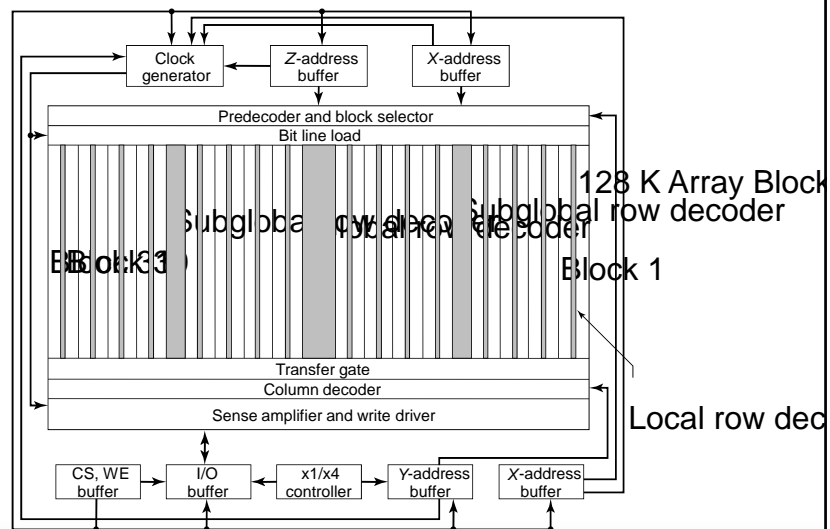


© Digital Integrated Circuits<sup>2nd</sup>

[Hirose90]

Memories


## Contents-Addressable Memory

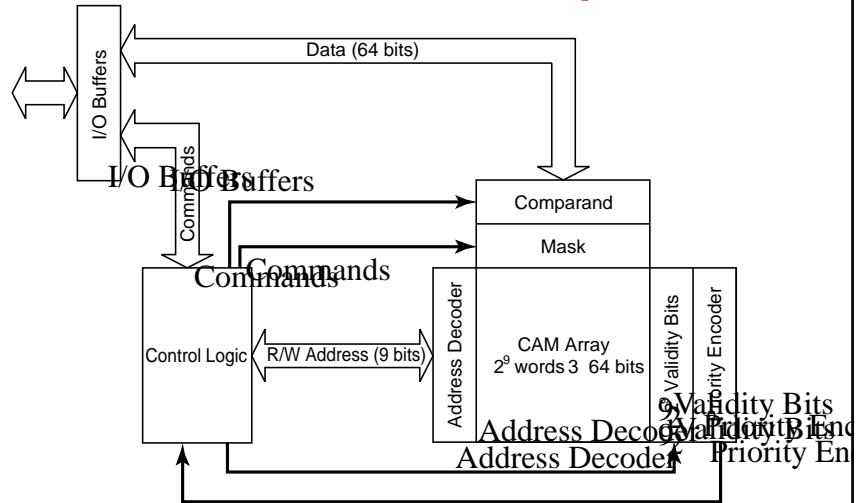


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Memory Timing: Approaches

 

 **DRAM Timing**  
**Multiplexed Addressing**




**SRAM Timing**  
**Self-timed**

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## Read-Only Memory Cells

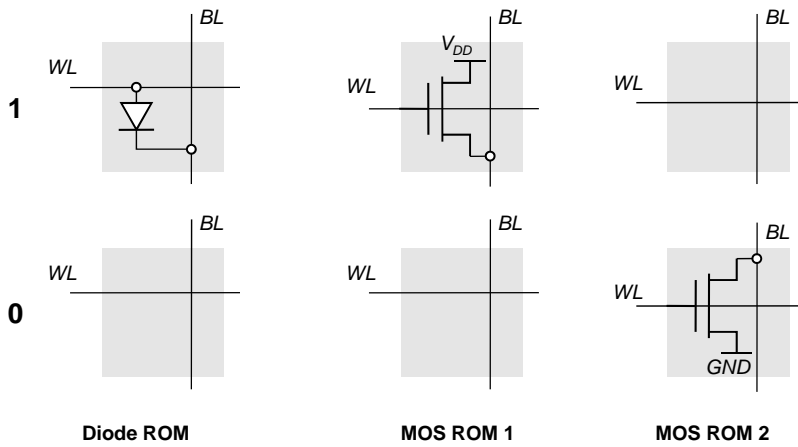

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## MOS OR ROM

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## MOS NOR ROM

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## MOS NOR ROM Layout

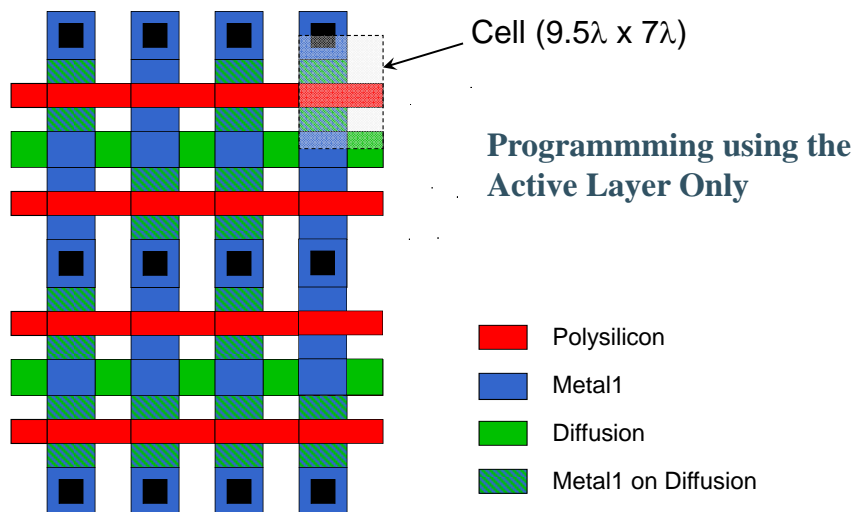


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## MOS NOR ROM Layout

Cell ( $11\lambda \times 7\lambda$ )

 


Programmming using  
the Contact Layer Only

- Polysilicon
- Metal1
- Diffusion
- Metal1 on Diffusion

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## MOS NAND ROM

 


All word lines high by default with exception of selected row

© Digital Integrated Circuits<sup>2nd</sup>

Memories




## MOS NAND ROM Layout

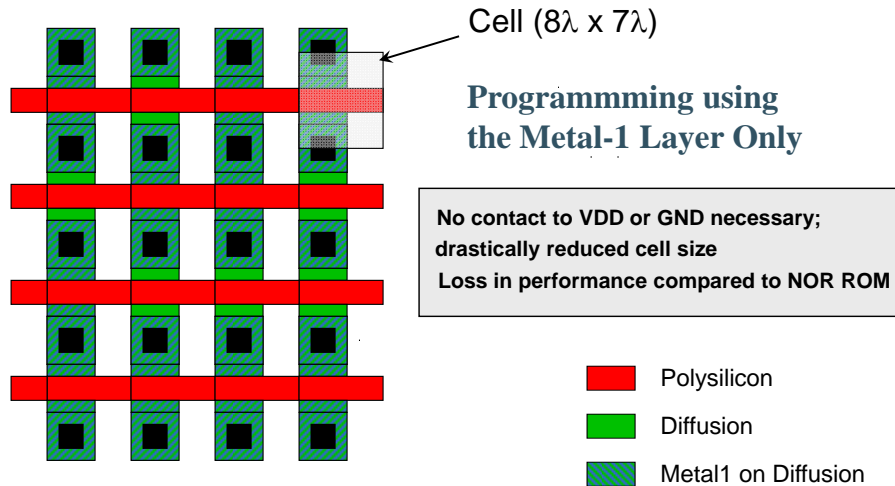

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## NAND ROM Layout

 


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Equivalent Transient Model for MOS NOR ROM

Model for NOR ROM

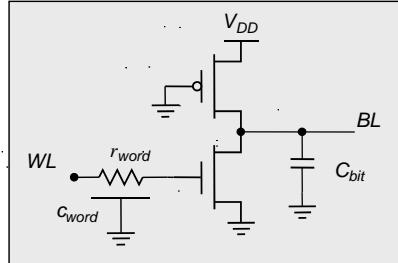


- Word line parasitics
  - Wire capacitance and gate capacitance
  - Wire resistance (polysilicon)
- Bit line parasitics
  - Resistance not dominant (metal)
  - Drain and Gate-Drain capacitance

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Equivalent Transient Model for MOS NAND ROM

Model for NAND ROM

 


- Word line parasitics
  - Similar to NOR ROM
- Bit line parasitics
  - Resistance of cascaded transistors dominates
  - Drain/Source and complete gate capacitance


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Decreasing Word Line Delay

 

 
(a) Driving the word line from both sides



(b) Using a metal bypass

(c) Use silicides


## Precharged MOS NOR ROM

 


**PMOS precharge device can be made as large as necessary, but clock driver becomes harder to design.**

## Non-Volatile Memories

### The Floating-gate transistor (FAMOS)

 

Device cross-section

 


Schematic symbol

© Digital Integrated Circuits<sup>2nd</sup>

Memories


### Floating-Gate Transistor Programming

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## A "Programmable-Threshold" Transistor

 


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## FLOTOX EEPROM

 

FLOTOX transistor

 


Fowler-Nordheim  
 $I$ - $V$  characteristic

© Digital Integrated Circuits<sup>2nd</sup>


Memories

## EEPROM Cell

 


Absolute threshold control  
is hard  
Unprogrammed transistor  
might be depletion  
⇒ **2 transistor cell**

## Flash EEPROM

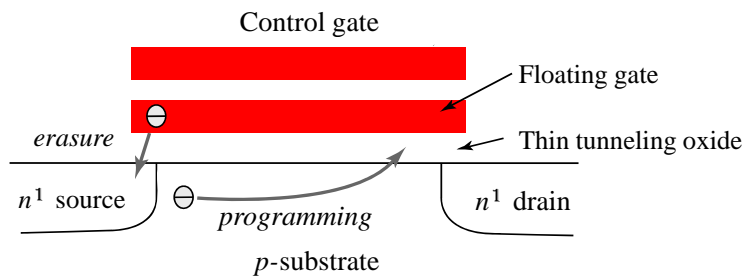

Many other options ...

## Cross-sections of NVM cells

 

**Flash**



**EPROM**

© Digital Integrated Circuits<sup>2nd</sup>

*Courtesy Intel*

Memories

  
## Basic Operations in a NOR Flash Memory—Erase



© Digital Integrated Circuits<sup>2nd</sup>

Memories

 
## Basic Operations in a NOR Flash Memory— Write



© Digital Integrated Circuits<sup>2nd</sup>

Memories
 
## Basic Operations in a NOR Flash Memory— Read





© Digital Integrated Circuits<sup>2nd</sup>

Memories



## NAND Flash Memory

  


© Digital Integrated Circuits<sup>2nd</sup>

Courtesy Toshiba

Memories

## NAND Flash Memory

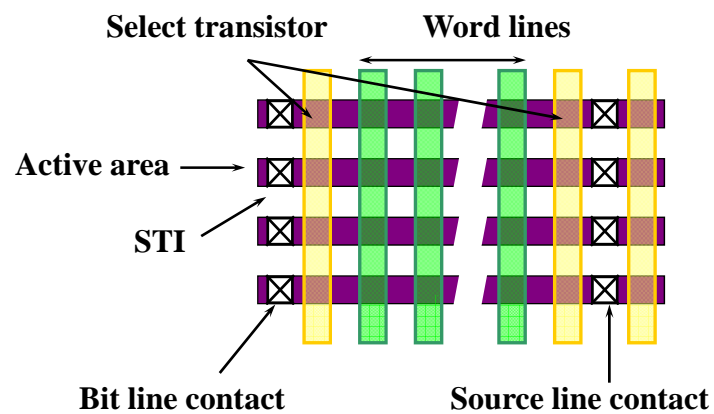

© Digital Integrated Circuits<sup>2nd</sup>

Courtesy Toshiba

Memories

## Characteristics of State-of-the-art NVM

**Table 12-1** Comparison between nonvolatile memories ([Itoh01]).  
 $V_{DD} = 3.3$  or  $5$  V;  $V_{PP} = 12$  or  $12.5$  V.

	Cell— Nr. of Transistors	Cell Area (ratio wrt EPROM)	Mechanism		External Power Supply		Program/ Erase Cycles
			Erase	Write	Write	Read	
MASK ROM	1 T (NAND)	0.35–5	—	—	—	$V_{DD}$	0
EPROM	1 T	1	UV Exposure	Hot electrons	$V_{PP}$	$V_{DD}$	~100
EEPROM	2 T	3–5	FN Tunneling	FN Tunneling	$V_{PP}$ (int)	$V_{DD}$	$10^4$ – $10^5$
Flash Memory	1 T	1–2	FN Tunneling	Hot electrons	$V_{PP}$	$V_{DD}$	$10^4$ – $10^5$
			FN Tunneling	FN Tunneling	$V_{PP}$ (int)	$V_{DD}$	$10^4$ – $10^5$

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Read-Write Memories (RAM)

### □ STATIC (SRAM)

**Data stored as long as supply is applied**

**Large (6 transistors/cell)**

**Fast**

**Differential**

### □ DYNAMIC (DRAM)

**Periodic refresh required**

**Small (1-3 transistors/cell)**


**Slower**

**Single Ended**

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## 6-transistor CMOS SRAM Cell

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## CMOS SRAM Analysis (Read)

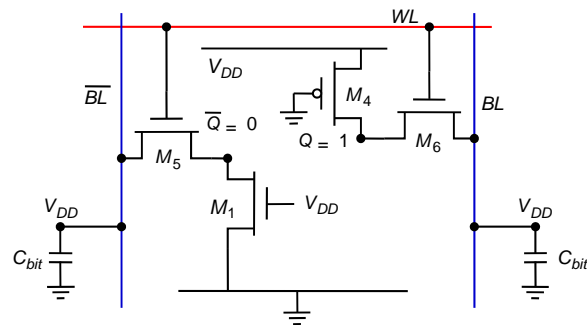


$$k_{n,M5} \left( (V_{DD} - \Delta V - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right) = k_{n,M1} \left( (V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$

$$\Delta V = \frac{V_{DSATn} + CR(V_{DD} - V_{Tn}) - \sqrt{V_{DSATn}^2(1 + CR) + CR^2(V_{DD} - V_{Tn})^2}}{CR}$$

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## CMOS SRAM Analysis (Read)

 


$$CR = \frac{W_1/L_1}{W_5/L_5}$$

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## CMOS SRAM Analysis (Write)

 


$$k_{n,M6} \left( (V_{DD} - V_{Tn}) V_Q - \frac{V_Q^2}{2} \right) = k_{p,M4} \left( (V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)$$

$$V_Q = V_{DD} - V_{Tn} - \sqrt{(V_{DD} - V_{Tn})^2 - 2 \frac{\mu_p}{\mu_n} PR \left( (V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)}$$

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## CMOS SRAM Analysis (Write)

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## 6T-SRAM — Layout

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Resistance-load SRAM Cell

 


Static power dissipation -- Want  $R_L$  large  
Bit lines precharged to  $V_{DD}$  to address  $t_p$  problem

## SRAM Characteristics

**Table 12-2** Comparison of CMOS SRAM cells used in 1-Mbit memory  
(from [Takada91])

	Complementary CMOS	Resistive Load	TFT Cell
Number of transistors	6	4	4 (+2 TFT)
Cell size	$58.2 \mu\text{m}^2$ (0.7- $\mu\text{m}$ rule)	$40.8 \mu\text{m}^2$ (0.7- $\mu\text{m}$ rule)	$41.1 \mu\text{m}^2$ (0.8- $\mu\text{m}$ rule)
Standby current (per cell)	$10^{-15}$ A	$10^{-12}$ A	$10^{-13}$ A

## 3-Transistor DRAM Cell

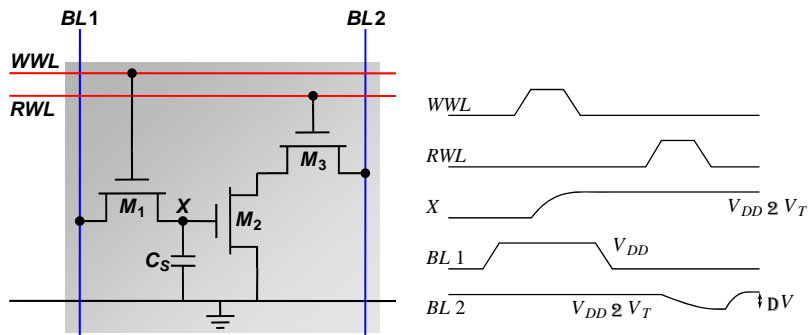


No constraints on device ratios  
 Reads are non-destructive  
 Value stored at node X when writing a "1" =  $V_{WWL} - V_{Tn}$

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## 3T-DRAM — Layout

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## 1-Transistor DRAM Cell

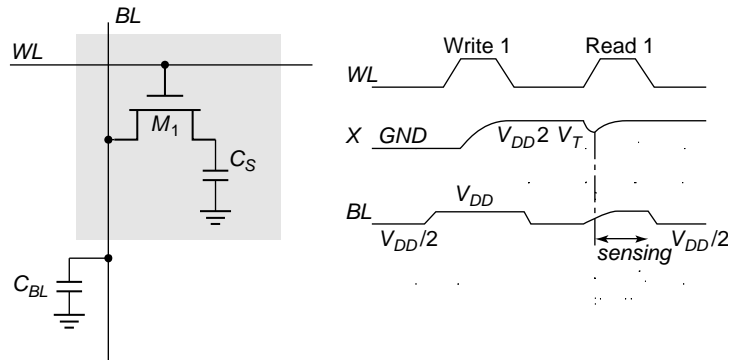

**Write:**  $C_S$  is charged or discharged by asserting WL and BL.

**Read:** Charge redistribution takes places between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = V_{BIT} - V_{PRE} \frac{C_S}{C_S + C_{BL}}$$

Voltage swing is small; typically around 250 mV.

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## DRAM Cell Observations


- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out.
- ❑ DRAM memory cells are single ended in contrast to SRAM cells.
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operations are necessary for correct operation.
- ❑ Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design.
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This charge loss can be circumvented by bootstrapping the word lines to a higher value than  $V_{DD}$

© Digital Integrated Circuits<sup>2nd</sup>

Memories




## Sense Amp Operation

 


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## 1-T DRAM Cell

 

**Cross-section**

 


**Layout**

Uses Polysilicon-Diffusion Capacitance  
Expensive in Area

© Digital Integrated Circuits<sup>2nd</sup>

Memories

 
## SEM of poly-diffusion capacitor 1T-DRAM




© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Advanced 1T DRAM Cells

 

**Trench Cell**

 


**Stacked-capacitor Cell**

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## Static CAM Memory Cell

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## CAM in Cache Memory

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Periphery

- ❑ Decoders
- ❑ Sense Amplifiers
- ❑ Input/Output Buffers
- ❑ Control / Timing Circuitry

## Row Decoders

Collection of  $2^M$  complex logic gates  
Organized in regular and dense fashion

### (N)AND Decoder

$$WL_0 = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

$$WL_{511} = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3 \bar{A}_4 \bar{A}_5 \bar{A}_6 \bar{A}_7 \bar{A}_8 \bar{A}_9$$


### NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{A_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$
 
## Hierarchical Decoders


*Multi-stage implementation improves performance*




© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Dynamic Decoders

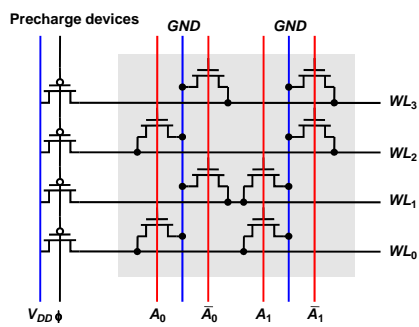

**2-input NOR decoder**

 


**2-input NAND decoder**

© Digital Integrated Circuits<sup>2nd</sup>

Memories
 
## 4-input pass-transistor based column decoder



**Advantages:** speed ( $t_{pd}$  does not add to overall memory access time)


Only one extra transistor in signal path

**Disadvantage:** Large transistor count

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## 4-to-1 tree based column decoder

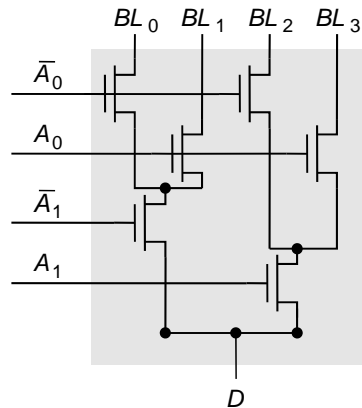

Number of devices drastically reduced

Delay increases quadratically with # of sections; prohibitive for large decoders

Solutions: buffers


progressive sizing

combination of tree and pass transistor approaches

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## Decoder for circular shift-register

 


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Sense Amplifiers

 


**Idea: Use Sense Amplifier**

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Differential Sense Amplifier

 


**Directly applicable to SRAMs**


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Differential Sensing – SRAM

 

(a) SRAM sensing scheme

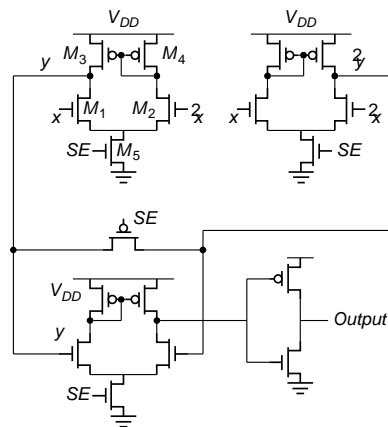


(b) two stage differential amplifier

© Digital Integrated Circuits<sup>2nd</sup>

Memories



## Latch-Based Sense Amplifier (DRAM)

 


Initialized in its meta-stable point with EQ  
Once adequate voltage gap created, sense amp enabled with SE  
Positive feedback quickly forces output to a stable operating point.


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Charge-Redistribution Amplifier

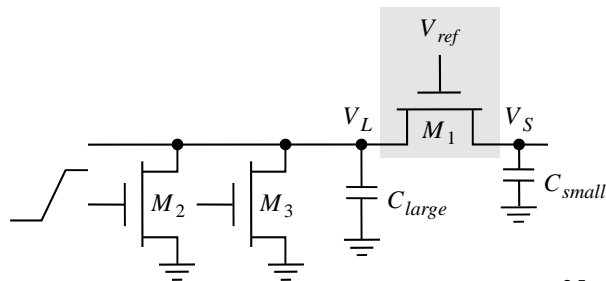


Concept

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

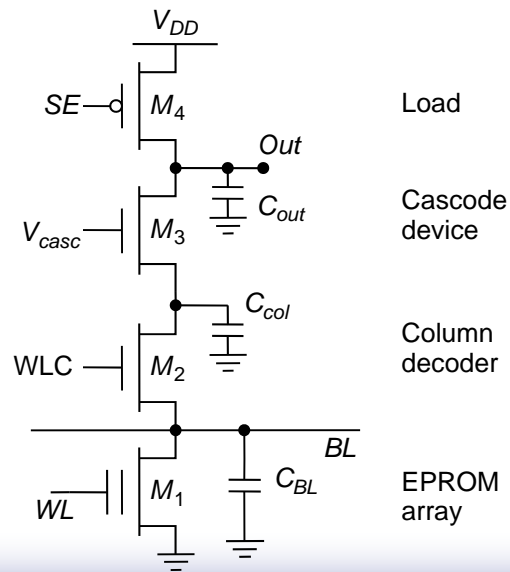
## Charge-Redistribution Amplifier— EPROM



© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Single-to-Differential Conversion

 


How to make a good  $V_{ref}$ ?

© Digital Integrated Circuits<sup>2nd</sup>

Memories

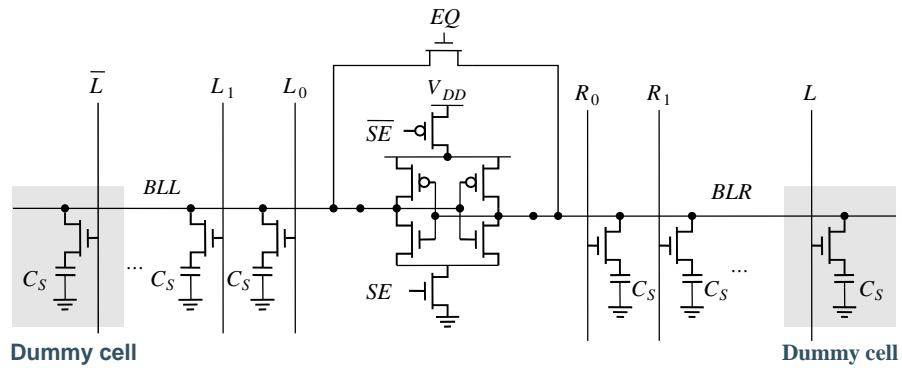
## Open bitline architecture with dummy cells



© Digital Integrated Circuits<sup>2nd</sup>

Memories


## DRAM Read Process with Dummy Cell

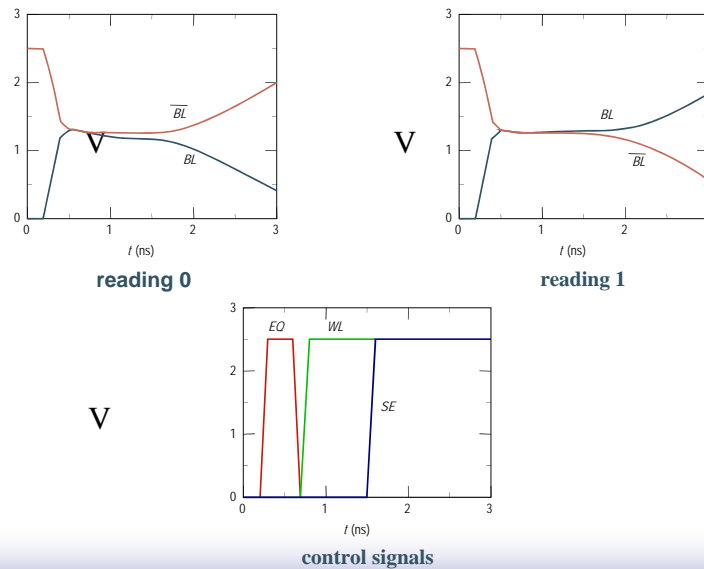


© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Voltage Regulator

 


### Equivalent Model

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## Charge Pump

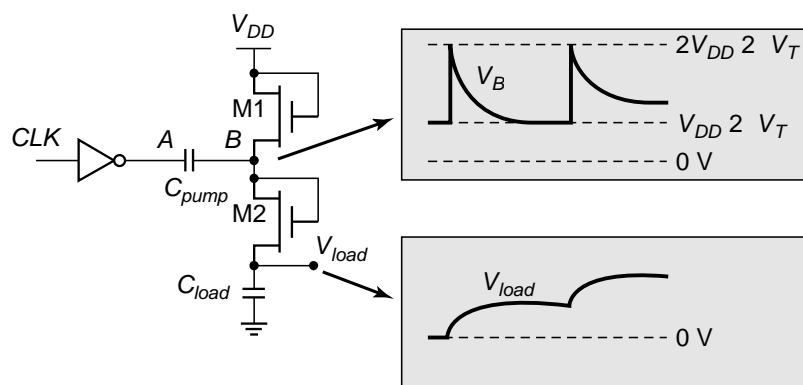

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## DRAM Timing

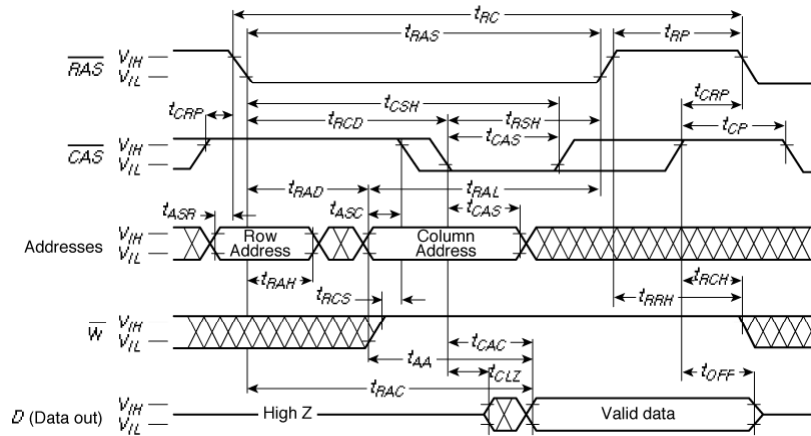

© Digital Integrated Circuits<sup>2nd</sup>

## Memories


## RDRAM Architecture

 

© Digital Integrated Circuits<sup>2nd</sup>

## Memories

## Address Transition Detection

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Reliability and Yield

- Semiconductor memories trade off noise-margin for density and performance



Highly Sensitive to Noise (Crosstalk, Supply Noise)

- High Density and Large Die size cause Yield Problems

$$Y = 100 \frac{\text{Number of Good Chips on Wafer}}{\text{Number of Chips on Wafer}}$$


$$Y = \left[ \frac{1 - e^{-AD}}{AD} \right]^2$$

Increase Yield using Error Correction and Redundancy

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Sensing Parameters in DRAM

 


© Digital Integrated Circuits<sup>2nd</sup>

From [Itoh01]

Memories


## Noise Sources in 1T DRam

 

© Digital Integrated Circuits<sup>2nd</sup>

Memories

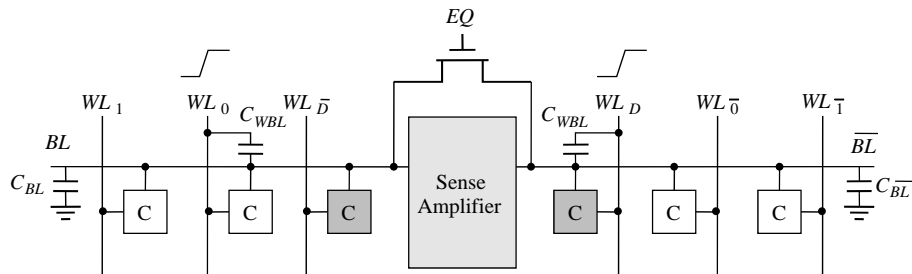
## Open Bit-line Architecture —Cross Coupling



© Digital Integrated Circuits<sup>2nd</sup>

## Memories

## Folded-Bitline Architecture

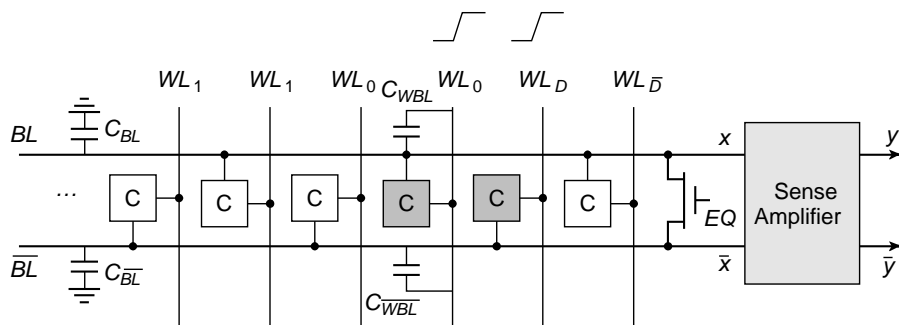


© Digital Integrated Circuits<sup>2nd</sup>


## Memories



## Transposed-Bitline Architecture

 

(a) Straightforward bit-line routing

 


(b) Transposed bit-line architecture

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Alpha-particles (or Neutrons)

 


**1 Particle ~ 1 Million Carriers**

© Digital Integrated Circuits<sup>2nd</sup>


Memories

## Yield

 

Yield curves at different stages of process maturity  
(from [Veendrick92])

## Redundancy

 

## Error-Correcting Codes

### Example: Hamming Codes

$P_1 P_2 B_3 P_4 B_5 B_6 B_7$

*e.g. B3 Wrong*

**with**

$$P_1 \oplus B_3 \oplus B_5 \oplus B_7 = 0$$

**1**

$$P_2 \oplus B_3 \oplus B_6 \oplus B_7 = 0$$


**1**

**= 3**


$$P_4 \oplus B_5 \oplus B_6 \oplus B_7 = 0$$

**0**

## Redundancy and Error Correction

 
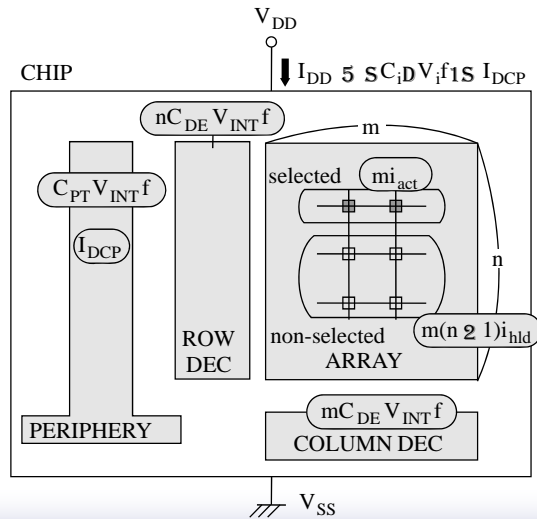
## Sources of Power Dissipation in Memories




© Digital Integrated Circuits<sup>2nd</sup>

From [Itoh00]

Memories

## Data Retention in SRAM

 


**SRAM leakage increases with technology scaling**

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Suppressing Leakage in SRAM

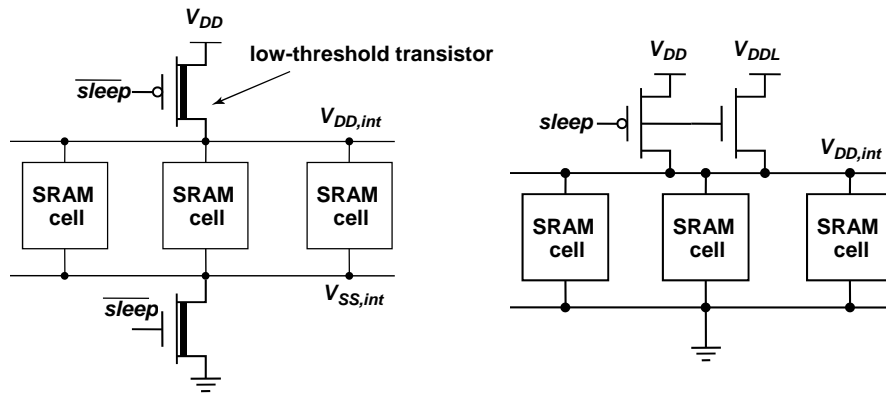


**Inserting Extra Resistance**

**Reducing the supply voltage**

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Data Retention in DRAM

 

© Digital Integrated Circuits<sup>2nd</sup>

From [Itoh00]

Memories

## Case Studies

- ❑ Programmable Logic Array
- ❑ SRAM
- ❑ Flash Memory

## PLA versus ROM

- ❑ **Programmable Logic Array**  
structured approach to random logic  
“two level logic implementation”  
NOR-NOR (product of sums)  
NAND-NAND (sum of products)

**IDENTICAL TO ROM!**

- ❑ **Main difference**  
ROM: fully populated  
PLA: one element per minterm


**Note:** Importance of PLA's has drastically reduced

1. slow
2. better software techniques (multi-level logic synthesis)

**But ...**

# Programmable Logic Array


## Pseudo-NMOS PLA

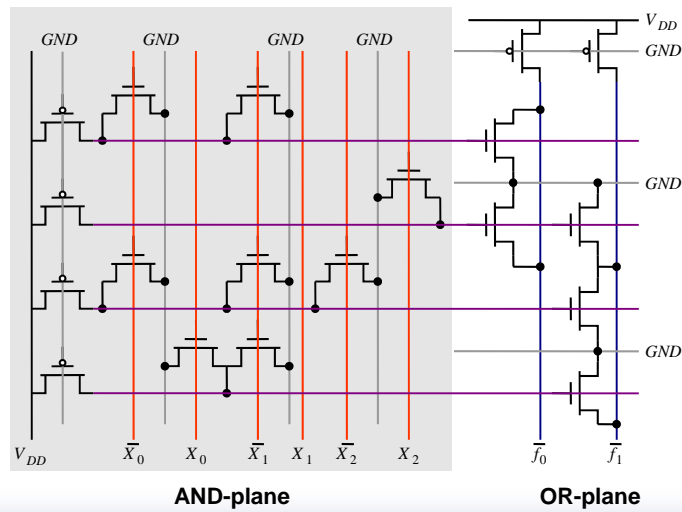

© Digital Integrated Circuits<sup>2nd</sup>

Memories


# Dynamic PLA

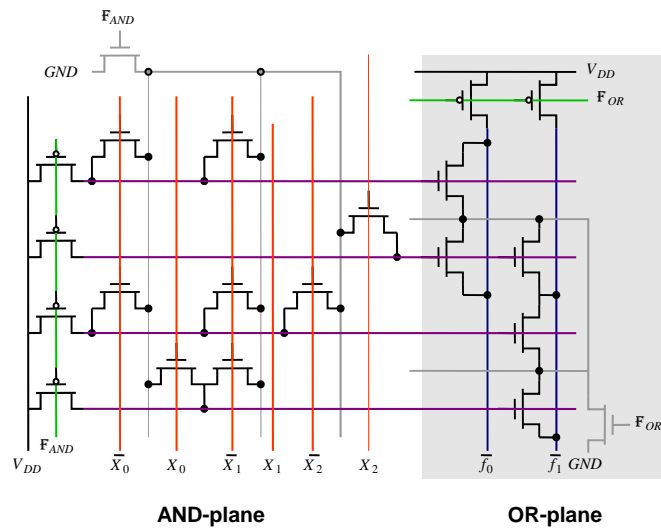

© Digital Integrated Circuits<sup>2nd</sup>

Memories

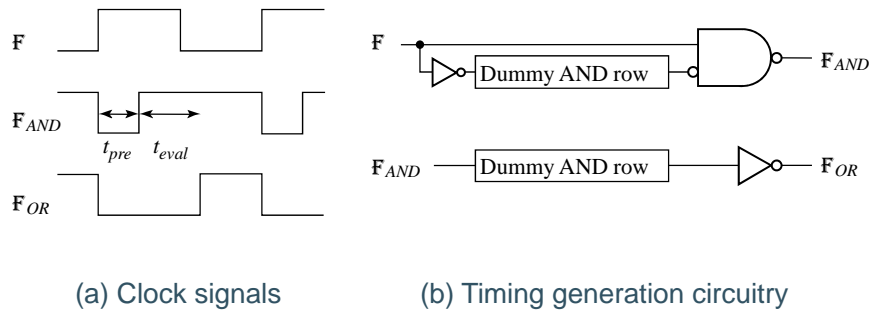
## Clock Signal Generation for self-timed dynamic PLA



© Digital Integrated Circuits<sup>2nd</sup>

Memories

## PLA Layout

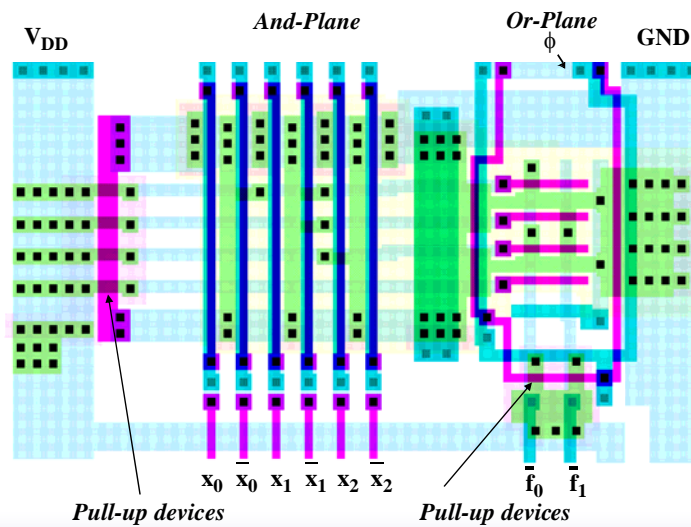


© Digital Integrated Circuits<sup>2nd</sup>

Memories



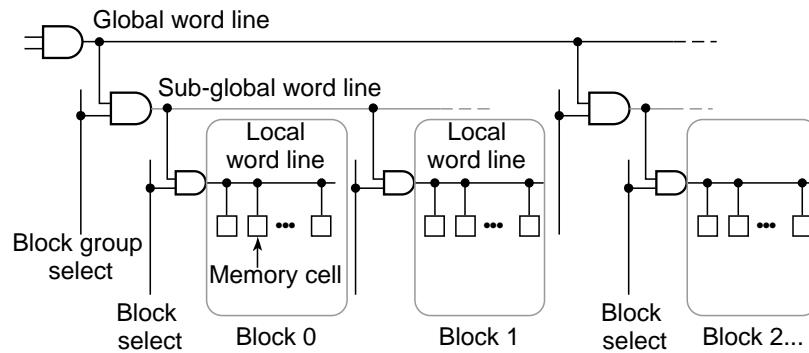
## 4 Mbit SRAM Hierarchical Word-line Architecture



© Digital Integrated Circuits<sup>2nd</sup>

Memories



## Bit-line Circuitry

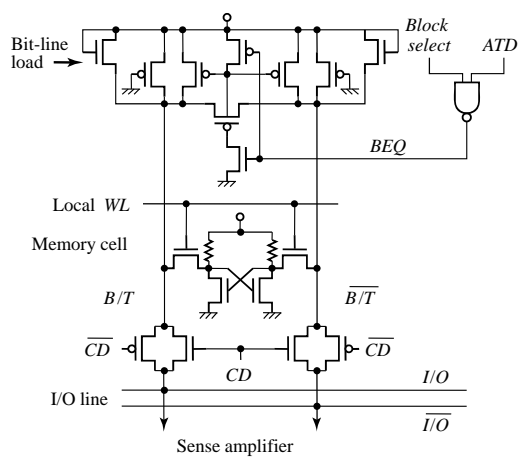

© Digital Integrated Circuits<sup>2nd</sup>

Memories


## Sense Amplifier (and Waveforms)

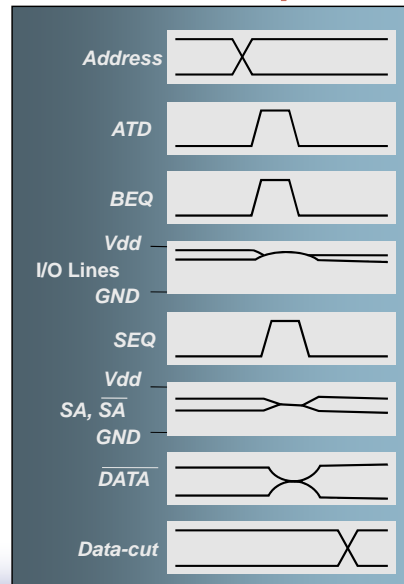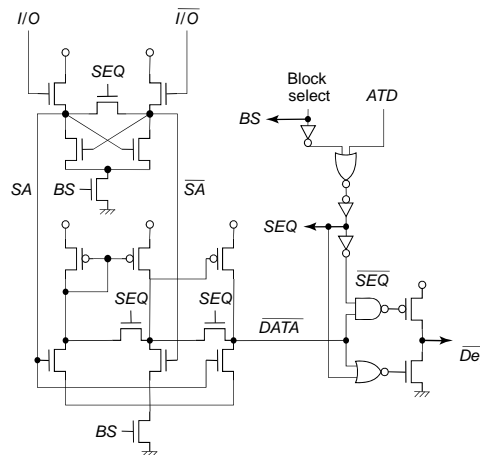

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## 1 Gbit Flash Memory

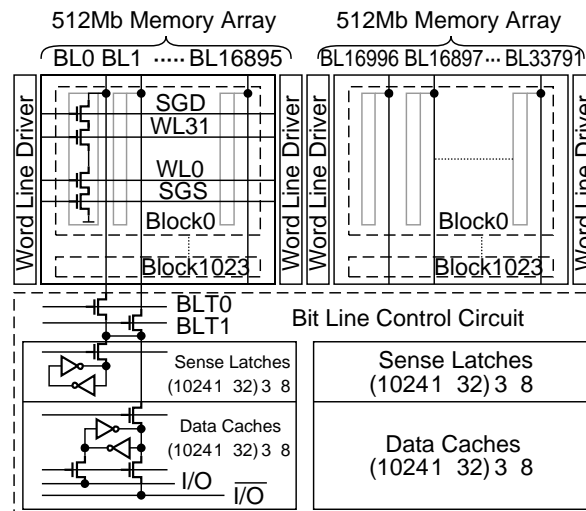


© Digital Integrated Circuits<sup>2nd</sup>

From [Nakamura02]

Memories

## Writing Flash Memory

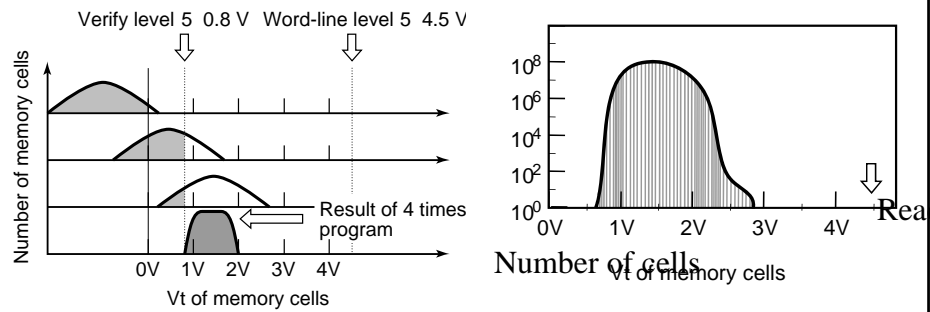

**Evolution of thresholds**


**Final Distribution**

© Digital Integrated Circuits<sup>2nd</sup>

From [Nakamura02]

Memories
 
## 125mm<sup>2</sup> 1Gbit NAND Flash Memory



© Digital Integrated Circuits<sup>2nd</sup>

From [Nakamura02]

Memories

## 125mm<sup>2</sup> 1Gbit NAND Flash Memory


❑ Technology	0.13μm p-sub CMOS triple-well 1poly, 1polycide, 1W, 2Al
❑ Cell size	0.077μm <sup>2</sup>
❑ Chip size	125.2mm <sup>2</sup>
❑ Organization	2112 x 8b x 64 page x 1k block
❑ Power supply	2.7V-3.6V
❑ Cycle time	50ns
❑ Read time	25μs
❑ Program time	200μs / page
❑ Erase time	2ms / block

© Digital Integrated Circuits<sup>2nd</sup>

From [Nakamura02]

Memories
 
## Semiconductor Memory Trends (up to the 90's)




Memory Size as a function of time: x 4 every three years

© Digital Integrated Circuits<sup>2nd</sup>

Memories

## Semiconductor Memory Trends (updated)

 


© Digital Integrated Circuits<sup>2nd</sup>

From [Itoh01]

Memories

## Trends in Memory Cell Area

 


© Digital Integrated Circuits<sup>2nd</sup>

From [Itoh01]

Memories

## Semiconductor Memory Trends

 

Technology feature size for different SRAM generations